


COMBINATION OF CAPACITORS

1. Three capacitors each of capacitance 9 pF are connected in series. The potential difference across the first capacitor if the combination is connected to a 120 V supply is:

(a) 20 V (b) 30 V (c) 40 V (d) 120 V


2. The equivalent capacitance between A and B in given figure is:

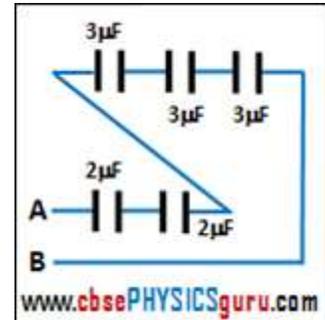(a) 0.5 μF (b) 1.5 μF (c) 13 μF (d) 4.5 μF




3. If N identical plates, each of area A and separation d are connected as shown in figure, the resultant capacitance is:

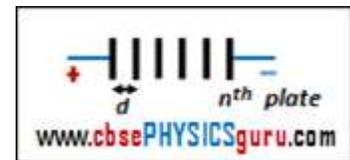(a) $\frac{\epsilon_0 A}{d(N+1)}$ (b) $\frac{\epsilon_0 A}{d(N-1)}$ (c) $\frac{\epsilon_0 A}{dN}$ (d) $\frac{\epsilon_0 AN}{d(N-1)}$




4. The total capacitance of the circuit between points A and B as shown in the figure is:

(a) 7 μF (b) 5 μF (c) 0.75 μF (d) 1.5 μF

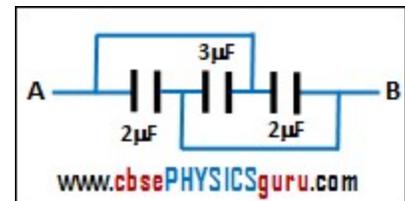


5. A capacitor half-filled with a dielectric constant 4 as shown in figure has a capacitance of 10 μF . Its capacitance without the dielectrics will be:

(a) 8 μF (b) 6 μF (c) 4 μF (d) 2 μF

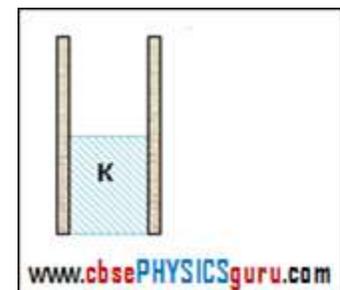


6. A capacitor is made of a flat plate of area A and second plate having a stair like structure as shown in figure. The width of each stair is $A/3$ and height is d . The capacitance of the system is:

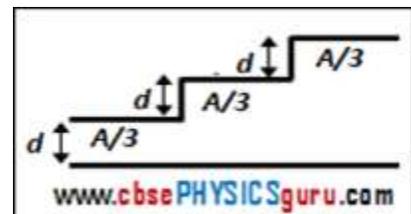(a) $\frac{5\epsilon_0 A}{18d}$ (b) $\frac{9\epsilon_0 A}{16d}$ (c) $\frac{11\epsilon_0 A}{15d}$ (d) $\frac{11\epsilon_0 A}{18d}$



7. Two dielectric slabs of dielectric constants K_1 and K_2 have been filled in between the plates of a capacitor as shown in figure. The capacitance of the capacitor is:

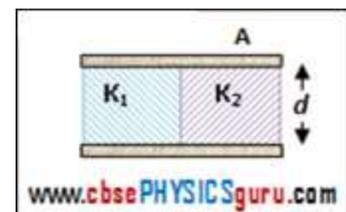(a) $\frac{\epsilon_0 A}{d} (K_1 + K_2)$ (b) $\frac{\epsilon_0 A}{2d} (K_1 + K_2)$ (c) $\frac{2\epsilon_0 A}{d} (K_1 + K_2)$ (d) $\frac{\epsilon_0 AK_1K_2}{2d(K_1 + K_2)}$




8. Series equivalent of two capacitors of equal capacitances is C_1 and their parallel equivalent is C_2 . The ratio C_1/C_2 is:

(a) $1/4$ (b) $1/3$ (c) $1/2$ (d) $2/5$


9. Two parallel plate capacitors X and Y as shown in figure, have the same area of plates and same separation between them. X has air between the plates while Y contains a dielectric medium of $K = 4$. The potential differences between the plates of X and Y are respectively:

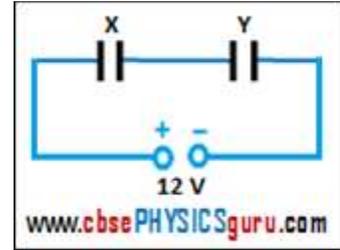(a) 6 V, 6 V (b) 8.4 V, 3.6 V (c) 9.6 V, 2.4 V (d) 10 V, 2 V




10. Three identical capacitors C_1 , C_2 and C_3 of capacitance $6 \mu\text{F}$ each are connected to a 12 V battery as shown in the figure. The charge on each capacitor is:

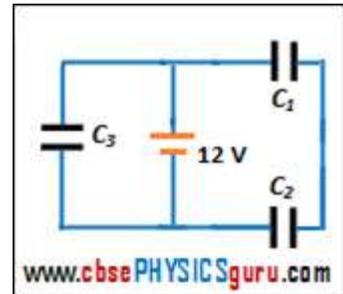(a) $q_1 = 36 \mu\text{C}$, $q_2 = 36 \mu\text{C}$, $q_3 = 36 \mu\text{C}$ (b) $q_1 = 72 \mu\text{C}$, $q_2 = 72 \mu\text{C}$, $q_3 = 36 \mu\text{C}$ (c) $q_1 = 18 \mu\text{C}$, $q_2 = 18 \mu\text{C}$, $q_3 = 36 \mu\text{C}$ (d) $q_1 = 36 \mu\text{C}$, $q_2 = 36 \mu\text{C}$, $q_3 = 72 \mu\text{C}$




11. Calculate the potential difference across the capacitor C_2 in the circuit shown in the figure. Given potential at A is 90 V, $C_1 = 20 \mu\text{F}$, $C_2 = 30 \mu\text{F}$, $C_3 = 15 \mu\text{F}$:


(a) 20 V (b) 30 V (c) 45 V (d) 60 V

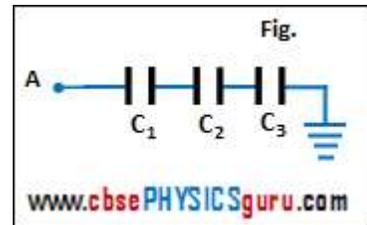

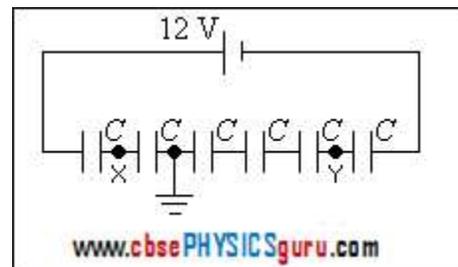12. The potential of points X and Y respectively are:
(a) 4 V, -2 V (b) -6 V, 2 V (c) 2 V, -6 V (d) -3 V, 6 V



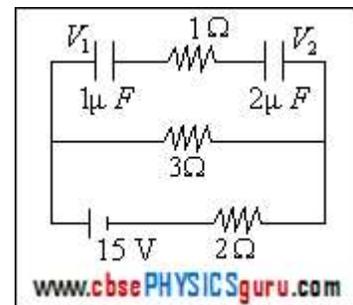13. The values of V_1 and V_2 respectively are:
(a) 3 V, 6 V (b) 6 V, 3 V (c) 3 V, 3 V (d) 2 V, 1 V



14. In the circuit shown, (i) A current of 0.9 Amp flows through $2\ \Omega$ resistor when steady state is reached (ii) A potential drop of 4.2 V appears across the resistance of $2.8\ \Omega$ (iii) A potential drop of 1.8 V appears across the capacitor C (iv) A potential drop of 4.2 V appears across the capacitor C. The correct alternative is:
(a) i, ii, iii (b) i, ii, iv (c) ii, iii, iv (d) i, iii, iv

