


SERIES AND PARALLEL COMBINATION OF RESISTORS

1. Three resistors draw currents of 2 A, 3 A and 6 A respectively when connected in turn across a battery. What will be the current drawn if these resistors are connected in series across the same battery?


(a) 1 A (b) 2 A (c) 3 A (d) 11 A

2. In the two circuits shown in the figure:

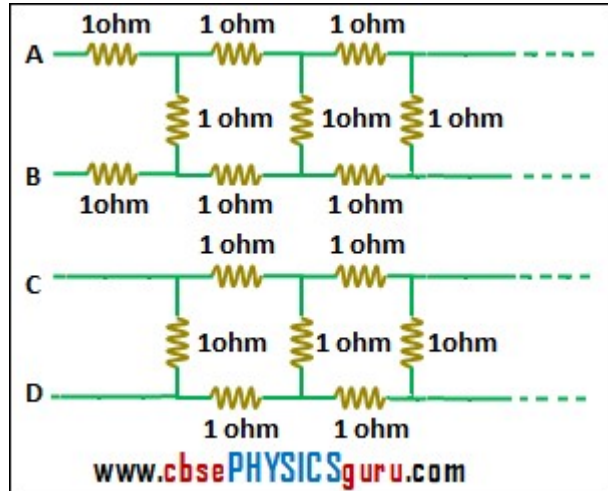(a) $R_{AB} = \sqrt{3} + 1$, $R_{CD} = \sqrt{3} - 1$ (b) $R_{AB} = \sqrt{3} + 1$,
 $R_{CD} = \sqrt{3} + 1$ (c) $R_{AB} = \sqrt{3} - 1$, $R_{CD} = \sqrt{3} + 1$ (d)
 $R_{AB} = \sqrt{3} + 2$, $R_{CD} = \sqrt{3} + 1$




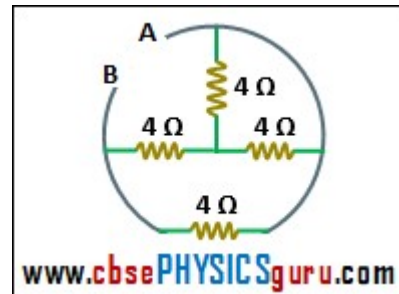3. Four resistances each of 4Ω are connected in the circuit as shown in figure. The equivalent resistance between A and B is:
 (a) 1.2Ω (b) 2.4Ω (c) 3.6Ω (d) 6Ω



4. What is the equivalent resistance between points X and Y in figure when the key K is (i) open (ii) closed?

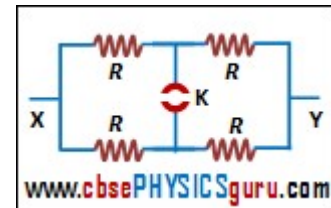(a) R, R (b) R, R/2 (c) R/2, R/2 (d) 2R, R



5. A circular ring of negligible resistance is used to connect four resistors of resistances $6R$, $6R$, $6R$ and R as shown in the figure. Find the equivalent resistance between points A & B.

(a) R (b) 2R (c) 3R (d) 4R




6. A wire of resistance 15Ω is gradually stretched to double its original length. It is then cut into two equal parts. These parts are then connected, in parallel across a 3.0 volt battery. The current drawn from the battery is:

(a) 0.1 A (b) 0.2 A (c) 0.3 A (d) 0.4 A


7. Calculate the current shown by the ammeter A in the circuit diagram shown in figure:

(a) 2 A (b) 4 A (c) 5 A (d) 7 A

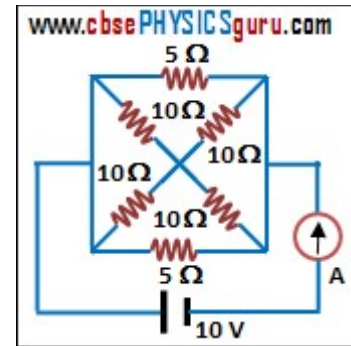


8. Six resistors, each of value 4Ω , are joined together in a circuit as shown in the figure. Calculate equivalent resistance across the points A and B:

(a) 2Ω (b) 4Ω (c) 8Ω (d) 10Ω

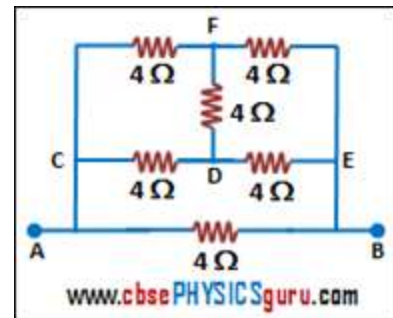


9. A potential difference of 2 volt is applied between the points A and B as shown in the network drawn in the figure. Calculate equivalent resistance of the network across the point A and B, and the magnitude of current flowing in the arms AFCEB. Given that $R = 2\text{ ohm}$:

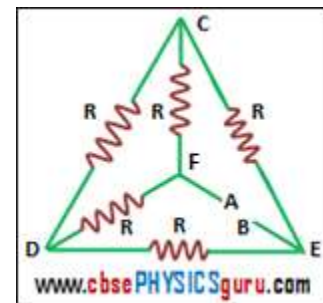(a) 2Ω , 0.5A (b) 4Ω , 0.5 A (c) 8Ω , 1 A (d) 10Ω , 2 A




10. Calculate the current drawn from the battery in the network shown in the figure exercise:

(a) 2 A (b) 4 A (c) 5 A (d) 8 A

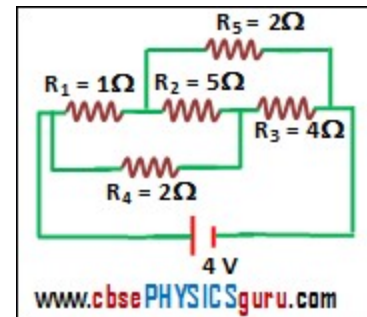


11. Potential difference across the capacitor in steady state will be:

(a) 2 V (b) 6 V (c) 8 V (d) 12 V

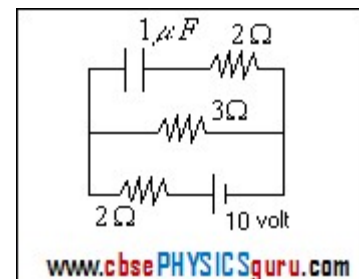


12. When a current of 0.5A is passed through two resistances in series, the potential difference between the ends of the series arrangement is 12.5V . On connecting them in parallel and passing the current of 1.5A , the potential difference between their ends is 6V , the two resistances are:
 (a) $12\ \Omega$, $13\ \Omega$ (b) $16\ \Omega$, $9\ \Omega$ (c) $15\ \Omega$, $10\ \Omega$ (d) $20\ \Omega$, $5\ \Omega$

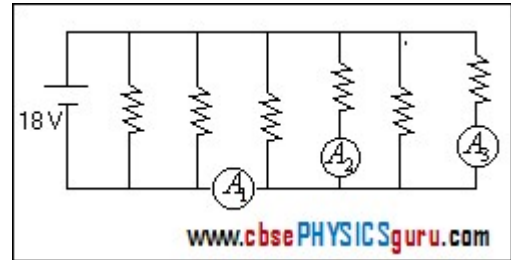
13. Six resistances each of $6\ \Omega$ are connected to an 18V battery as shown. The readings of ammeters A_1 , A_2 and A_3 will be respectively:
 (a) 12 A , 3 A , 3 A (b) 12 A , 9 A , 6 A (c) 3 A , 6 A , 9 A (d) 3 A , 6 A , 12 A



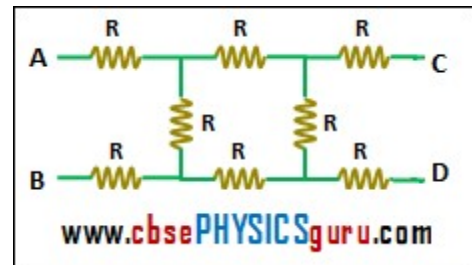
14. Figure shows a network of resistances. The ratio of the resistance between points A and C and that between A and D of the network is:
 (a) $13:14$ (b) $4:11$ (c) $9:11$ (d) $11:12$



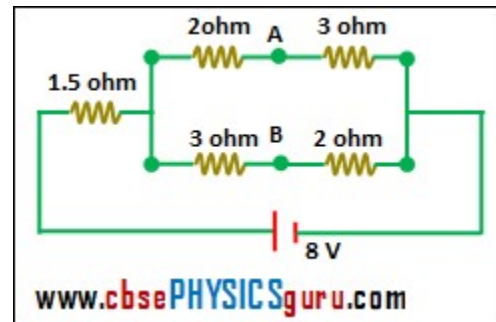15. The potential difference between A and B is:
 (a) 1 V (b) 2 V (c) 3 V (d) -1 V



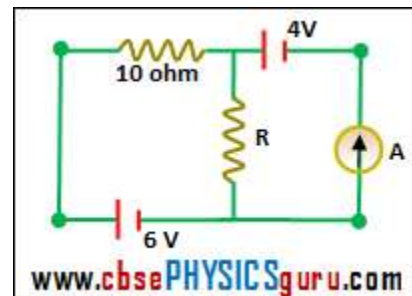16. The reading of the ammeter A is zero. The value of the resistor R is:
 (a) $8\ \Omega$ (b) $10\ \Omega$ (c) $20\ \Omega$ (d) $40\ \Omega$



17. Two resistances $3\ \Omega$ and $6\ \Omega$ are connected in parallel and a $4\ \Omega$ resistance is connected in series. The current through $3\ \Omega$ resistance is 0.8 A . Then the potential drop through $4\ \Omega$ resistance is:
 (a) 9.6 V (b) 2.6 V (c) 4.8 V (d) 1.2 V
18. Two resistors of resistances $200\text{ k}\Omega$ and $1\text{ M}\Omega$ respectively form a potential divider with outer junctions maintained at potentials of $+3\text{ V}$ and -15 V . Then, the potential at the junction between the resistors is:
 (a) 0 V (b) $+1\text{ V}$ (c) -12 V (d) $+12\text{ V}$