
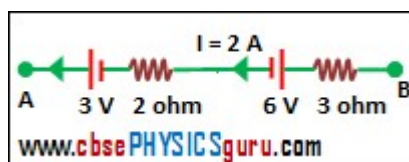


EMF AND COMBINATION OF CELLS

- The emf of a cell is e and its internal resistance r . Its terminals are connected to a resistance R . The potential difference between the terminals is 1.6 V for $R = 4 \Omega$ and 1.8 V for $R = 9 \Omega$. Then:
(a) $e = 1 \text{ V}$, $r = 1 \Omega$ (b) $e = 2 \text{ V}$, $r = 1 \Omega$ (c) $e = 1 \text{ V}$, $r = 2 \Omega$ (d) $e = 1 \text{ V}$, $r = 1.5 \Omega$
- When a current of 2 A flows in a battery from negative to positive terminal, the potential difference across it is 12 V. If a current of 3 A flowing in the opposite produces a potential difference of 15 V, the emf battery is:
(a) 10.6 V (b) 13.2 V (c) 15.5 V (d) 16.0
- A battery of emf e has an internal resistance r . A resistance R is connected to the terminals of the battery. A current I is drawn from the battery. V is the terminal potential difference. If R alone is gradually reduced to zero, which of the following best describes I and V ?
(a) I approaches zero, V approaches e (b) I approaches e/r , V approaches zero (c) I approaches e/r , V approaches e (d) I approaches infinity, V approaches e
- A battery of emf e produces currents I_1 and I_2 when connected to external resistances R_1 and R_2 respectively. The internal resistance of the battery is:
(a) $\frac{I_1 R_2 - I_2 R_1}{I_2 - I_1}$ (b) $\frac{I_1 R_2 - I_2 R_1}{I_2 + I_1}$ (c) $\frac{I_1 R_1 - I_2 R_2}{I_2 - I_1}$ (d) $\frac{I_1 R_1 + I_2 R_2}{I_2 + I_1}$
- A battery of emf 8 V with internal resistance 0.5Ω is being charged by a 120 V dc supply using a series resistance of 15.5Ω . The terminal voltage of the battery is:
(a) 9.5 V (b) 10.5 V (c) 11.5 V (d) 5.5 V
- The box shown in diagram has five batteries, each of emf e and internal resistance r , connected randomly in series. This setup is connected across a resistor R . The maximum and minimum possible values of currents in the resistor R respectively are:
(a) $\frac{e}{R+5r}$, $\frac{5e}{R+5r}$ (b) $\frac{5e}{R+5r}$, $\frac{e}{R+5r}$ (c) $\frac{5e}{5R+r}$, $\frac{5e}{R+5r}$ (d) $\frac{5e}{R+r}$, $\frac{5e}{R+5r}$
- The number of cells, each of emf 1.5 volt and internal resistance 0.5 ohm that must be joined in series with a resistance of 20 ohm so as to send a current of 0.6 ampere through the circuit is:
(a) 2 (b) 8 (c) 10 (d) 12
- 32 cells each of emf 3 V are connected in series and kept in a box. Externally, the combination shows an emf of 84 V. The number of cells reversed in the connection is:
(a) 0 (b) 2 (c) 4 (d) 8
- N identical cells, each of emf e and internal resistance r , are joined to form a closed circuit. One cell X is joined with reverse polarity. The potential difference across each except X is:
(a) $\frac{2e}{N}$ (b) $\frac{(N-1)e}{N}$ (c) $\frac{(N-2)e}{N}$ (d) $\frac{Ne}{N-1}$
- Three similar cells, each of emf 2 V and internal resistance $r \Omega$ send the same current through an external resistance of 2Ω , when connected in series or in parallel. The current flowing through the external resistance is:
(a) 1 A (b) 1.5 A (c) 2 A (d) 0.75 A
- The potential difference ($V_A - V_B$) between the points A and B in the given figure is:
(a) -13 V (b) +13 V (c) +16 V (d) -19 V

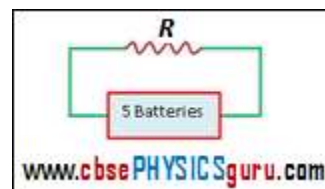

12. Two batteries of emfs 2 V and 1 V of internal resistances 1 Ω and 2 Ω respectively are connected in parallel. The effective emf of the combination is:
(a) $4/3$ V (b) $5/3$ V (c) 2 V (d) $5/2$ V
13. n cells each of emf e and internal resistance r send the same current through an external resistance R whether the cells are connected in series or in parallel. Then:
(a) $R = r$ (b) $R = r/n$ (c) $r = R/n$ (d) $R = n^2r$
14. 3 cells each of emf 4 V and internal resistance of 1 Ω are connected in parallel to a load resistor of 1.75 Ω . Then the current through the load resistor is:
(a) 2 A (b) 2.5 A (c) 1 A (d) 1.5 A
15. The plot of the variation of potential difference across a combination of three identical cells in series, versus current is shown in figure. The emf and internal resistance of each cell used are respectively:
(a) 1.5 V, 1.5 Ω (b) 6 V, 2 Ω (c) 2 V, 2 Ω (d) 1 V, 1 Ω

