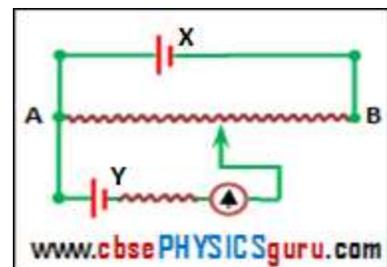


## METER BRIDGE AND POTENTIOMETER

- Two resistances are connected in two gaps of meter-bridge. The balance point is 20 cm from the zero end. A resistance of  $15\ \Omega$  is connected in series with the smaller of the two. The null point shifts to 40 cm. The value of the smaller resistance in ohm is:  
(a) 3 (b) 6 (c) 9 (d) 12
- Resistors X and Y connected in the gaps of the meter-bridge. The balancing point is obtained  $\frac{1}{3}$  m from the zero end. If a  $6\ \Omega$  resistance is connected in series with X, the balance point shifts to  $\frac{2}{3}$  m from same end. X and Y are:  
(a) 4, 2 (b) 2, 4 (c) 3, 5 (d) 3, 6
- A resistance of  $2\ \Omega$  is connected across the gap of a meter-bridge and an unknown resistance, greater than  $2\ \Omega$ , is connected across the other gap. When these resistances are interchanged, the balance point shifts by 20 cm. Neglecting any correction, the unknown resistance is:  
(a)  $3\ \Omega$  (b)  $4\ \Omega$  (c)  $5\ \Omega$  (d)  $6\ \Omega$
- The percentage error in measuring resistance with a meter-bridge can be minimized by adjusting the balancing point close to:  
(a) 0 cm (b) 20 cm (c) 50 cm (d) 100 cm
- A meter bridge is balanced with a  $20\ \Omega$  resistance in the left gap and  $30\ \Omega$  in the right gap. If the  $20\ \Omega$  resistance is now shunted by another  $20\ \Omega$  resistance, the shift in the null point is:  
(a) 15 m towards right (b) 25 m towards left (c) 15 m towards right (d) 15 m towards left
- A potentiometer wire of length 200 cm has a resistance of  $20\ \Omega$ . It is connected in series with a resistance  $10\ \Omega$  and a battery of emf 6 V having negligible internal resistance. A source of 2.4 V is balanced a length L of the potentiometer wire. The value of L is:  
(a) 100 cm (b) 120 cm (c) 110 cm (d) 140 cm.
- A potentiometer wire of length 100 cm has a resistance of 10 ohm. It is connected in series with a resistance and a cell of emf 2 volt and of negligible internal resistance. A source of emf 10 mV is balanced against a length 40 cm of the potentiometer wire. The value of external resistance is:  
(a)  $790\ \Omega$  (b)  $890\ \Omega$  (c)  $990\ \Omega$  (d)  $1050\ \Omega$
- The potential gradient along the length of a uniform wire is 10 volt per metre. B and C are two points at 30 cm and 70 cm on a metre scale along the wire: The potential difference between B and C will be:  
(a) 3 volt (b) 4 volt (c) 7 volt (d) 4 volt.
- Figure shows a potentiometer using a cell X of 2 V and internal resistance  $0.5\ \Omega$  connected to a wire AB. A standard cell Y of a constant emf of 1.02 V gives a balance point at 51 cm of the wire. When Y is replaced by a cell of emf  $\epsilon$ , the balance point is obtained 75 cm. The value of  $\epsilon$  is:  
(a) 1.25 V (b) 1.5 V (c) 1.75 V (d) 2.0 V
- A potentiometer wire, 10 m long, has a resistance of  $40\ \Omega$ . It is connected in series with a resistance box and 2 V storage cell. If the potential gradient along the wire is  $0.1\ \text{mV/cm}$ , the resistance unplugged in the box is:  
(a)  $260\ \Omega$  (b)  $860\ \Omega$  (c)  $860\ \Omega$  (d)  $760\ \Omega$
- In a potentiometer experiment, the balancing with a cell is at length 240 cm. On shunting the cell with a resistance of  $2\ \Omega$ , the balancing length becomes 120 cm. The internal resistance of the cell is:



**(a)**  $2 \Omega$  **(b)**  $4 \Omega$  **(c)**  $0.5 \Omega$  **(d)**  $1 \Omega$

12. A potentiometer has uniform potential gradient. The specific resistance of the material of the potentiometer wire is  $10^{-7} \Omega \text{ m}$  and the current passing through it is  $0.1 \text{ A}$ , cross section of the wire is  $10^{-6} \text{ m}^2$ . The potential gradient along the potentiometer wire is:  
**(a)**  $10^{-4} \text{ V/m}$  **(b)**  $10^{-6} \text{ V/m}$  **(c)**  $10^{-2} \text{ V/m}$  **(d)**  $10^{-8} \text{ V/m}$
13. In a potentiometer experiment, when three cells A, B and C are connected in series the balancing length is found to be  $740 \text{ cm}$ . If A and B are connected in series balancing length is  $440 \text{ cm}$  and for B and C connected in series that is  $540 \text{ cm}$ . Then the emf of  $\epsilon_A$ ,  $\epsilon_B$  and  $\epsilon_C$  are respectively (in volts):  
**(a)**  $1.0, 1.2$  and  $1.5$  **(b)**  $1.0, 2.0$  and  $3.0$  **(c)**  $1.5, 2.0$  and  $3.0$  **(d)**  $1.5, 2.5$  and  $3.5$
14. In an experiment with potentiometer, a cell of emf  $1.25 \text{ V}$  gives a balance point at  $35 \text{ cm}$  length of the wire. If the cell is replaced by another cell, the balance point shift to  $63 \text{ cm}$ . The emf of the second cell is:  
**(a)**  $3.25 \text{ V}$  **(b)**  $2.5 \text{ V}$  **(c)**  $2.25 \text{ V}$  **(d)**  $2 \text{ V}$
15. The accurate measurement of emf can be obtained using:  
**(a)** multimeter **(b)** voltmeter **(c)** voltmeter **(d)** potentiometer